ngspice01

antoine.remy99


March 12 2020

1 GSchem

I started this project by creating a gschem document to create my circuit I used one voltage generator and 2 resistor :

- -Resistor 1 as a value of 27Ω
- -Resistor 2 as a value of $127.\Omega$
- -Voltage generator as a value of $54\mathrm{V}$.

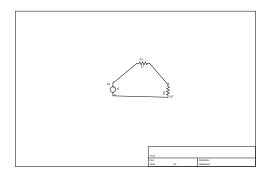And I linked all the component to obtain this :



I finally transformed the .sch into a .net by using gnetlist.

the file net file was:

* Spice netlister for gnetlist

V1 1 0 54

R2 0 2 127


R1 1 2 27

.END


2 NGspice

After exporting the .sch into a .net using gnetlist.

I used ng spice to calculate the different voltage of all the resistors by using command : -tran 5 1 -plot "1" -plot "2" as show below:

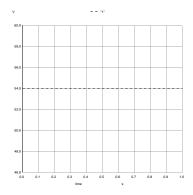

Resistor 1

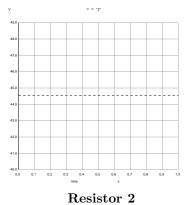

3 Conclusion

This work allow me to learn how to create electrical circuit in GSchem and to evaluate them using NGspice.